

1.

$$(1) v_i(t) = L \frac{di(t)}{dt} + Ri(t), \quad v_o(t) = Ri(t)$$

$$(2) V_i(\omega) = (j\omega L + R)I(\omega), \quad V_o(\omega) = RI(\omega)$$

$$(3) H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{R}{(j\omega L + R)} = \frac{1}{(1 + j\omega L/R)} = \frac{1}{\sqrt{1 + (\omega L/R)^2}} e^{-j \tan^{-1}(\omega L/R)}$$

$$(4) h(t) = F^{-1}[H(\omega)] = \left[\frac{R}{L} \cdot \frac{1}{(R/L + j\omega)} \right] = \frac{R}{L} e^{-\frac{R}{L}t} u(t)$$

(5) $v_i(t) = u(t)$ なので,

$$v_o(t) = h(t) * u(t) = \left[\int_0^t \frac{R}{L} e^{-\frac{R}{L}x} dx \right] u(t) = \left(1 - e^{-\frac{R}{L}t} \right) u(t)$$

2.

(1)

$$Y(\omega) = \frac{1}{20 + j\omega} = \frac{1}{\sqrt{400 + \omega^2}} \exp \left[-j \tan^{-1} \left(\frac{\omega}{20} \right) \right]$$

$$(2) e(t) = \sin 20t = \cos \left(20t - \frac{\pi}{2} \right) = \operatorname{Re} \left[\exp \left\{ j \left(20t - \frac{\pi}{2} \right) \right\} \right]$$

$$i(t) = \operatorname{Re} \left[Y(20) \exp \left\{ j \left(20t - \frac{\pi}{2} \right) \right\} \right] = \operatorname{Re} \left[\frac{1}{20\sqrt{2}} e^{-j\frac{\pi}{4}} e^{j(20t - \frac{\pi}{2})} \right] = \frac{1}{20\sqrt{2}} \cos \left(20t - \frac{3\pi}{4} \right)$$

(3) $e(t) = 1 + \cos 20t + \cos 60t$

$$\begin{aligned} i(t) &= \operatorname{Re} \left[Y(0) \exp(j0) + Y(20) \exp(j20t) + Y(60) \exp(j60t) \right] \\ &= \frac{1}{20} + \operatorname{Re} \left[\frac{1}{20\sqrt{2}} e^{-j\frac{\pi}{4}} \exp(j20t) \right] + \operatorname{Re} \left[\frac{1}{20\sqrt{10}} \exp \left\{ -j \tan^{-1}(3) \right\} \exp(j60t) \right] \\ &= \frac{1}{20} + \frac{1}{20\sqrt{2}} \cos \left(20t - \frac{\pi}{4} \right) + \frac{1}{20\sqrt{10}} \cos \left(60t - \tan^{-1}(3) \right) \end{aligned}$$

(4) $e(t) = u(t)$ この回路のインパルス応答 $y(t)$ は

$$y(t) = F^{-1}[Y(\omega)] = F^{-1} \left[\frac{1}{20 + j\omega} \right] = e^{-20t} u(t)$$

$$i(t) = y(t) * u(t)$$

$$= \left[\int_0^t e^{-20x} dx \right] \cdot u(t) = \left[-\frac{1}{20} e^{-20x} \right]_0^t \cdot u(t) = \frac{1}{20} (1 - e^{-20t}) \cdot u(t)$$